

---

# **INTRODUCTION TO POWER ELECTRONICS**

**3<sup>rd</sup> Edition – Type V 0121**

---

© **hps SystemTechnik**

Lehr- + Lernmittel GmbH

Altdorfer Strasse 16  
88276 Berg / Germany

Phone: + 49 751 / 5 60 75 80  
Telefax: + 49 751 / 5 60 75 17  
Internet: <http://www.hps-systemtechnik.com>  
E-mail: [export@hps-systemtechnik.com](mailto:export@hps-systemtechnik.com)

**Order no.: V 0121**

All rights reserved. No part of this publication may be reproduced, transmitted, stored in a retrieval system, nor translated into any human or computer language, in any form or by any means, electronic, mechanical, magnetic, optical, chemical, manual or otherwise, without the prior permission of hps SystemTechnik.

0.6.1

---

## Contents

|                                                                                    |            |
|------------------------------------------------------------------------------------|------------|
| <b>1. Introduction .....</b>                                                       | <b>1</b>   |
| <b>2. Uncontrolled rectifiers .....</b>                                            | <b>5</b>   |
| 2.1 The uncontrolled single-pulse mid-point circuit M1U .....                      | 5          |
| 2.2 The uncontrolled double-pulse bridge circuit B2U .....                         | 15         |
| 2.3 The uncontrolled three-pulse mid-point circuit M3U.....                        | 21         |
| 2.4 The uncontrolled six-pulse bridge circuit B6U.....                             | 27         |
| 2.5 Arithmetic average and rms value in uncontrolled rectifiers .....              | 33         |
| 2.6 Number of pulses and ripple in uncontrolled rectifiers .....                   | 39         |
| <b>3. Controlled rectifiers .....</b>                                              | <b>45</b>  |
| 3.1 The controlled single-pulse mid-point circuit M1C .....                        | 45         |
| 3.2 The controlled double-pulse bridge circuit B2C .....                           | 57         |
| 3.3 The phase gate control circuit .....                                           | 63         |
| 3.4 The semi-controlled double-pulse bridge circuit B2H.....                       | 69         |
| 3.5 The controlled three-pulse mid-point circuit M3C.....                          | 77         |
| 3.6 Inverter mode of the controlled three-pulse mid-point circuit M3C .....        | 87         |
| 3.7 The controlled six-pulse bridge circuit B6C.....                               | 95         |
| 3.8 Arithmetic average and rms value of the current in controlled rectifiers ..... | 103        |
| <b>4. AC converters .....</b>                                                      | <b>107</b> |
| 4.1 The controlled single-phase alternating circuit W1C.....                       | 107        |
| 4.2 The pulse group control.....                                                   | 115        |

|                                                              |            |
|--------------------------------------------------------------|------------|
| <b>5. Direct current converters .....</b>                    | <b>119</b> |
| 5.1 The pulse width modulation .....                         | 119        |
| 5.2 Pulse width modulated direct DC converter with GTO ..... | 125        |
| 5.3 DC/DC converters.....                                    | 131        |
| 5.4 MOS-FET H-bridge with offset pulse width modulation..... | 145        |
| <b>6. Inverters.....</b>                                     | <b>171</b> |
| 6.1 The H-bridge as an inverter .....                        | 171        |

## Solutions

|                                |             |
|--------------------------------|-------------|
| Uncontrolled rectifiers .....  | S 1 - S 12  |
| Controlled rectifiers .....    | S 13 - S 26 |
| AC converters .....            | S 7 - S 30  |
| Direct current converters..... | S 31 - S 46 |
| Inverters .....                | S 47 - S 50 |

## Appendix

|                                        |     |
|----------------------------------------|-----|
| List of abbreviations and symbols..... | A 1 |
| Required measuring equipment.....      | A 2 |

## Foil

|                                                 |     |
|-------------------------------------------------|-----|
| Front view of the POWER BOARD (Type 5125) ..... | F 1 |
|-------------------------------------------------|-----|