

Filter and Oscillator Circuits

1st Edition – Type V 0136



SystemTechnik

© hps SystemTechnik

Lehr- + Lernmittel GmbH

Altdorfer Strasse 16
88276 Berg / Germany

Phone: + 49 751 / 5 60 75 80
Telefax: + 49 751 / 5 60 75 17
Internet: www.hps-systemtechnik.com
E-mail: export@hps-systemtechnik.com

Order no.: V 0136

All rights reserved. No part of this publication may be reproduced, transmitted, stored in a retrieval system, nor translated into any human or computer language, in any form or by any means, electronic, mechanical, magnetic, optical, chemical, manual or otherwise, without the prior permission of hps SystemTechnik.

0.11.1



SystemTechnik

Training in Technology

Contents

1	Passive Filters	1
1.1	Theoretical Introduction	1
1.2	Low-pass Filter with RC Element	4
1.2.1	Basic principles	4
1.2.2	Limiting frequency of an RC low-pass filter 	5
1.3	High-pass Filter with RC Element	6
1.3.1	Basic principles	6
1.3.2	Limiting frequency of an RC high-pass filter 	7
1.4	Parallel Resonant Circuit with LCR Element	8
1.4.1	Basic principles	8
1.4.2	Resonant frequency and quality of an LCR parallel resonant circuit 	9
1.5	Series Resonant Circuit with LCR Element	10
1.5.1	Basic principles	10
1.5.2	Resonant frequency and quality of an LCR series resonant circuit 	11
2	Active Filters	12
2.1	Theoretical Introduction	12
2.2	1 st Order Low-pass Filter	13
2.2.1	Basic principles	13
2.2.2	Limiting frequency and gain of a 1 st order low-pass filter 	14
2.3	2 nd Order Low-pass Filter	15
2.3.1	Basic principles	15
2.3.2	Limiting frequency and gain of a 2 nd order low-pass filter 	16
2.4	3 rd Order Low-pass Filter  	18
2.5	4 th Order Low-pass Filter	20
2.6	1 st Order High-pass Filter	22
2.6.1	Basic principles	22
2.6.2	Limiting frequency and gain of a 1 st order high-pass filter 	23
2.7	2 nd Order High-pass Filter 	24
2.8	2 nd Order Bandpass Filter	26
2.8.1	Basic principles	26
2.8.2	Resonant frequency and quality of a 2 nd order bandpass filter 	27
2.9	Bandpass Filter with Variable Quality 	29
2.10	Notch Filter	30
2.10.1	Basic principles	30
2.10.2	Notch filter with variable quality 	31
2.11	All-pass Filter	32
2.11.1	Basic principles	32
2.11.2	Phase shifter with 1 st order low-pass filter 	33
2.11.3	Variable phase shifter 	34
3	Digital Filters	35
3.1	Theoretical Introduction	35
3.1.1	Capacitors in sync	35
3.1.2	Universal Dual Filter	37
3.1.3	What you need to know about handling the Universal Dual Filter!	37
3.2	2 nd Order Filter Circuits	39
3.2.1	2 nd order low-pass filter, bandpass filter and notch filter  	39
3.2.2	2 nd order bandpass filter with variable quality  	41
3.3	Bandpass Filter in Cascade Circuit 	43

4 Oscillators	45
4.1 Theoretical Introduction	45
4.2 Crystal Oscillators	47
4.2.1 Basic principles	47
4.2.2 Output frequency of a crystal oscillator 	48
4.3 CMOS Oscillators 	49
4.4 Meissner Oscillators	50
4.4.1 Meissner oscillator in base circuit 	50
4.4.2 Meissner oscillator in emitter circuit 	51
4.5 Hartley Oscillator 	52
4.6 Colpitts Oscillator 	53
4.7 Voltage/frequency Converters	54
4.7.1 Basic principles	54
4.7.2 Characteristic of a voltage/frequency converter 	55
4.8 Astable Multivibrator	56
4.8.1 Basic principles	56
4.8.2 Dimensioning of an astable multivibrator 	57
4.9 RC Generator with Operational Amplifier 	58
4.10 Squarewave/delta Generator 	59
4.11 Sawtooth Generator 	60
5 Appendix	A1
5.1 Important Notes for the Measurements	A1
5.2 Measuring Instruments and Generators Used	A1
Solutions	L1